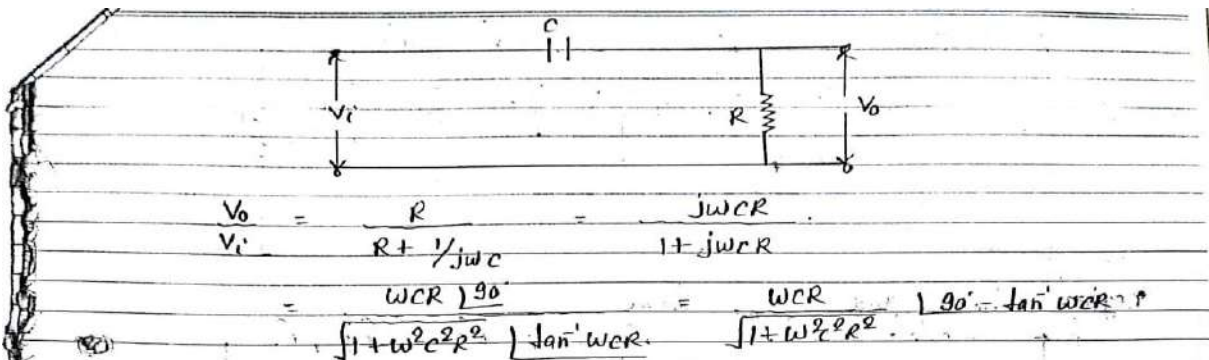


SET-A

SOLUTION-1


* R-C phase shift osc^x → -
 generating low freqⁿ oscillation L-C osc^x can't be used for


∴ generating low freqⁿ signal requires high value of L
 means it requires bulky and massive inductors, which
 is expensive. So for generating audio freqⁿ signal,
 R-C osc^x are used. They have good freqⁿ response
 and better stability.




∴ $\phi = 90^\circ - \tan^{-1} wCR$
 for $R \rightarrow \infty$, $\phi = 90^\circ$

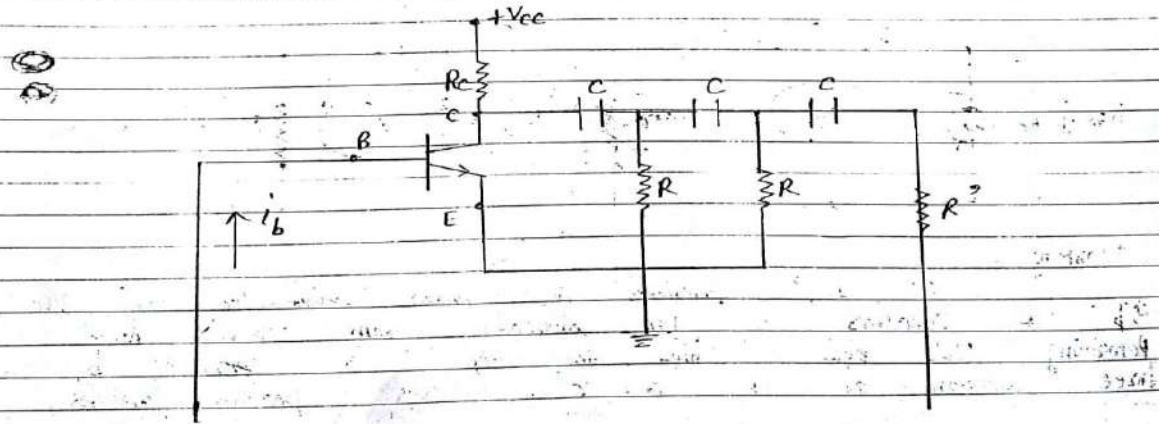but it is impractical, R and C are selected that phi is nearly equals to 60°. So total phase shift required is 180°. So three such sections are connected in cascade.




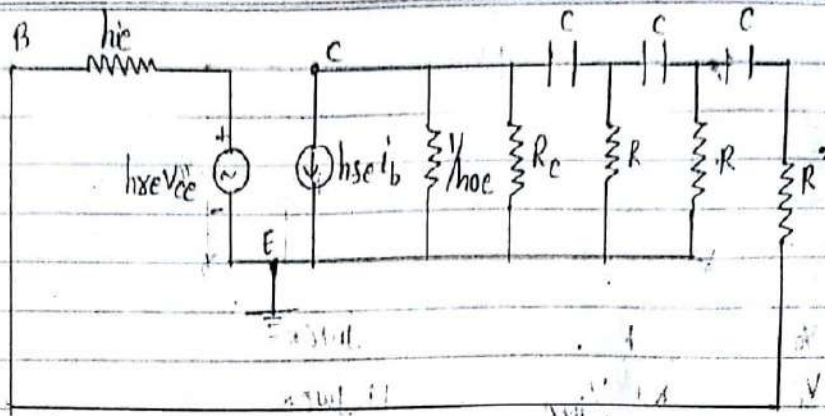

neglect h_{oe} and h_{ce} term

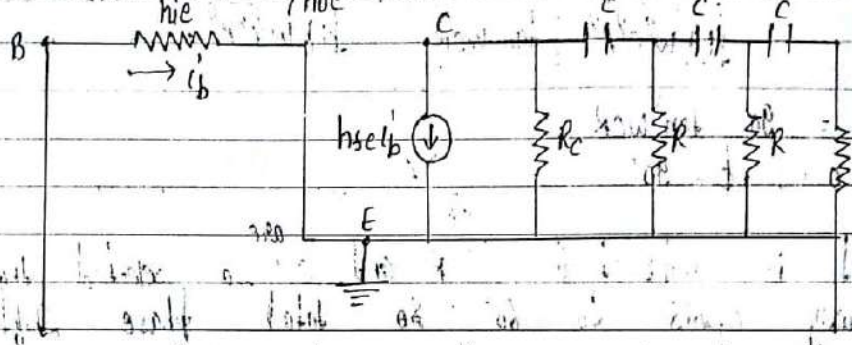

Convert norton form in thevin form

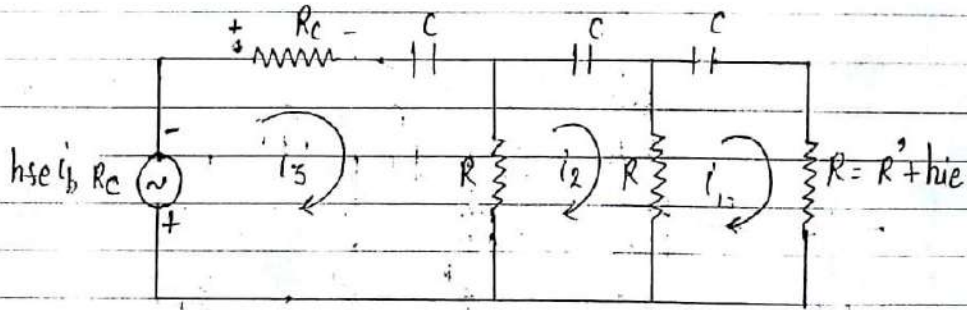

Working →

CE amp^x provides a phase shift of 180° , so o/p at collector is 180° shifted from i/p at base. Remaining 180° phase shift to o/p is provided by three sections of R and C. every section provides

KVL for loop-①

$$i_1 (1/j\omega C + R) + (i_1 - i_2)R = 0$$

$$\Rightarrow i_1 (1/j\omega C + 2R) + i_2 (-R) = 0 \quad \text{(i)}$$

KVL for loop-②

$$i_2 (1/j\omega C) + (i_2 - i_1)R + (i_2 - i_3)R = 0 \quad \text{(ii)}$$

KVL for loop-③

$$\Rightarrow h_{se} i_1 R_c + i_3 (R_c + 1/j\omega C) + (i_3 - i_2)R = 0$$

$$i_1 (h_{se} R_c) + i_2 (-R) + i_3 (R_c + 1/j\omega C + R) = 0 \quad \text{(iii)}$$

Writing eqⁿ (i), (ii), (iii) in matrix form \rightarrow

$$\begin{bmatrix} 1/j\omega C + 2R & -R & 0 \\ -R & 1/j\omega C + 2R & -R \\ h_{se} R_c & -R & 1/j\omega C + R_c + R \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = 0$$

Putting determinant of matrix to zero \rightarrow

$$\Rightarrow (1/j\omega C + 2R) \{ (1/j\omega C + 2R)(1/j\omega C + R + R_c) - R^2 \} - (-R) \{ (-R) \}$$

$$(1/j\omega C + R + R_c) - (-R)(h_{se} + R_c) \} = 0$$

equating imaginary part to zero -

$$6R^2 - \frac{1}{\omega^2 C^2} + 4R_c R = 0$$

$$\Rightarrow \omega = \frac{1}{R_c \sqrt{\beta + 4a}} \quad (a = R_c/R)$$

Now equating real part to zero


$$h_{se} = 23 + 29 \frac{R}{R_c} + 4 \frac{R_c}{R}$$

$$= 23 + 29/a + 4a$$

OR

SOLUTION-1

i) Voltage-series s/b →

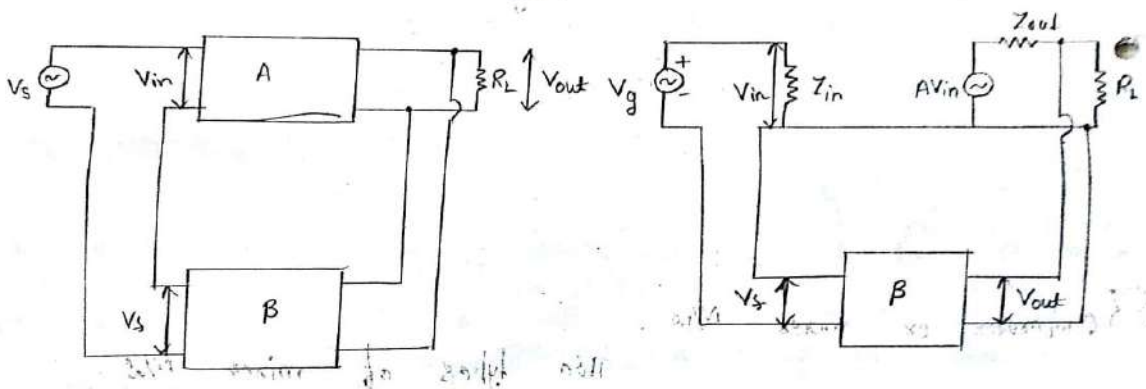

$$a) \quad I_{in} = \frac{V_{in}}{Z_{in}}$$

$$= \frac{V_g - V_s}{Z_{in}}$$

$$= \frac{V_g - \beta V_{out}}{Z_{in}} = \frac{V_g - \beta A V_{in}}{Z_{in}}$$

$$I_{in} Z_{in} = V_g - \beta A V_{in}$$

$$\frac{V_o}{I_{in}} = Z_{in} + A\beta Z_{in}$$

$$Z_{in,s} = Z_{in} (1 + A\beta)$$

$$b) \quad V_{out} = I_{out} Z_{out} + A V_{in}$$

$$= I_{out} Z_{out} - A V_o \quad (V_{in} = -V_o)$$

$$= I_{out} Z_{out} - A (\beta V_{out})$$

$$V_{out} + A\beta V_{out} = I_{out} Z_{out}$$

$$V_{out} (1 + A\beta) = I_{out} Z_{out}$$

$$\frac{V_{out}}{I_{out}} = \frac{Z_{out}}{1 + A\beta}$$

$$Z_{out,s} = \frac{Z_{out}}{1 + A\beta}$$

SOLUTION-2

(6) Effect of negative f/b on B.W.:

The voltage gain with f/b is given as

$$A_{vf} = \frac{A_v}{1 + A_v \beta} \approx \frac{1}{\beta} \quad \text{if } \beta A_v \gg 1 \quad \text{--- (1)}$$

when negative f/b is applied in an amp^{er},

of $(1+A\beta)$ while upper cut off freq. is raised by the same factor $(1+A\beta)$.

(i) Lower cut-off freq f_l : The voltage gain at a freq f in low freq. range of R-C coupled amp^r is given as.

$$A_{vL} = \frac{A_{vmid}}{1 - j \frac{f_l}{f}} \quad \text{--- (1)}$$

where f_l is the lower cut-off freq and $j = \sqrt{-1}$.

A_{vmid} = voltage gain in mid freq range
 A_{vL} = " " " at low " " "
 when negative f/b is applied

$$A_{vmp} = \frac{A_{vmf}}{1 + \beta A_{vmf}} = \frac{A_{vm}}{1 + \beta A_{vm}} \quad \text{--- (2)}$$

$$\text{and } A_{vLf} = \frac{A_{vL}}{1 + \beta A_{vL}} \quad \text{--- (3)}$$

Substituting the value of A_{vL} from eq (1) in eq (3).

$$A_{vLf} = \frac{A_{vmid}}{1 - j \frac{f_l}{f}} \cdot \frac{1}{1 + \beta \frac{A_{vmid}}{1 - j \frac{f_l}{f}}}$$

$$\text{OR } A_{vLf} = \frac{A_{vm}}{1 + \beta A_{vm}}$$

By dividing numerator and denominator by $1 + \beta A_{vm}$, the eqn may be re-written as

$$A_{vlf} = \frac{A_{vo} A_{vmf}}{1 - j f_i' / f} \quad (4)$$

where $A_{vmf} = \frac{A_{vm}}{1 + \beta |1 + \beta A_{vm}|}$ and $f_i' = f_i / (1 + \beta A_{vm})$ (5)

So, the midband amplification with flb A_{vmf} equals the midband amplification without flb divided by $1 + \beta A_{vm}$. Also the lower freq. with flb f_i' equals the lower cutoff freq. without flb f_i divided by the same factor $(1 + \beta A_{vm})$ i.e. lower cutoff freq. is reduced when negative flb is applied.

(iii) Upper cut-off frequency

The voltage gain at freq f in the high frequency range of RC coupled amp^r is given by

$$A_{vh} = \frac{A_{vm}}{1 + j f / f_2} \quad (6)$$

where f_2 = upper cutoff freq. without using flb.

A_{vm} - voltage gain in mid freq.

when negative ffb is applied

$$A_{v_{nf}} = \frac{A_{v_n}}{1 + \beta A_{v_n}} \quad \text{--- (2)}$$

Substituting the value of A_{v_n} from (1) to (2),

$$A_{v_{nf}} = \frac{A_{v_m}}{1 + jf/f_2} \cdot \frac{1 + \beta A_{v_m}}{1 + jf/f_2}$$


$$A_{v_{nf}} = \frac{A_{v_m}}{1 + \beta A_{v_m} + jf/f_2}$$

By dividing the numerator and denominator by $1 + \beta A_{v_m}$, the above eqn may be rewritten as

$$A_{v_{nf}} = \frac{A_{v_{mf}}}{1 + jf/f_2'} \quad \text{--- (3)}$$

where ~~$A_{v_{mf}} = A_v$~~
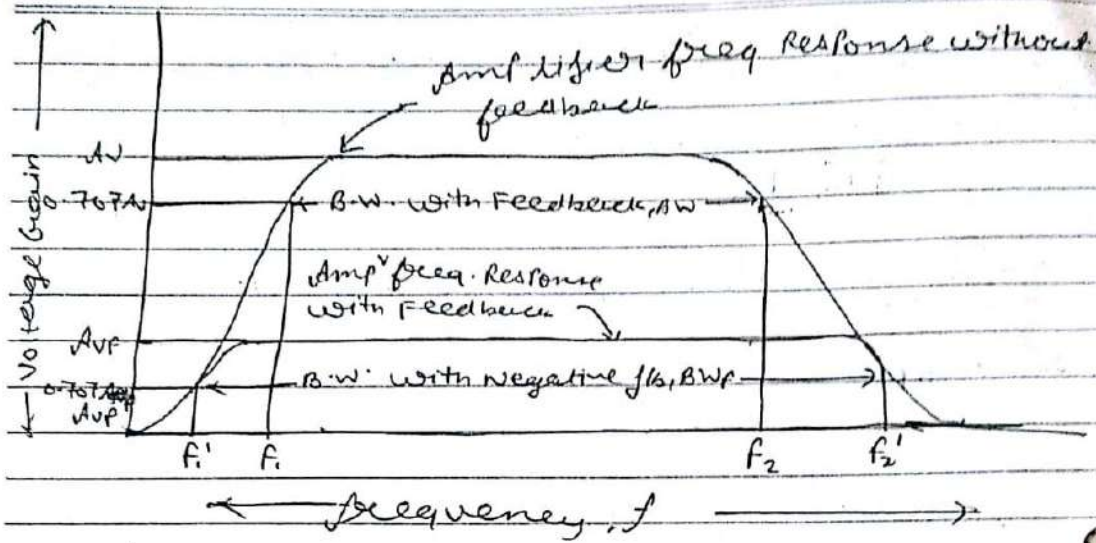
$$A_{v_{mf}} = \frac{A_{v_m}}{1 + \beta A_{v_m}} \quad \text{--- (4)}$$



* Amp^v Frequency Response with and without negative feedback →

Thus we see that upper cutoff freq. equals the corresponding cutoff freq. without f/b f_2 multiplied by the factor $(1 + \beta A_{vm})$ i.e. upper cutoff freq. is raised when -ive f/b is applied in an amp^v.

* Bandwidth → The B.W. with negative f/b is given as

$$BW_f = f_2' - f_1'$$

$$= f_2(1 + \beta A_{vm}) - f_1 \quad \text{--- (1)}$$


It's very clear that $(f_2' - f_1') > (f_2 - f_1)$

and hence B.W. of amplifier with f/b is greater than B.W. of amp^v without feedback.

OR


SOLUTION-2

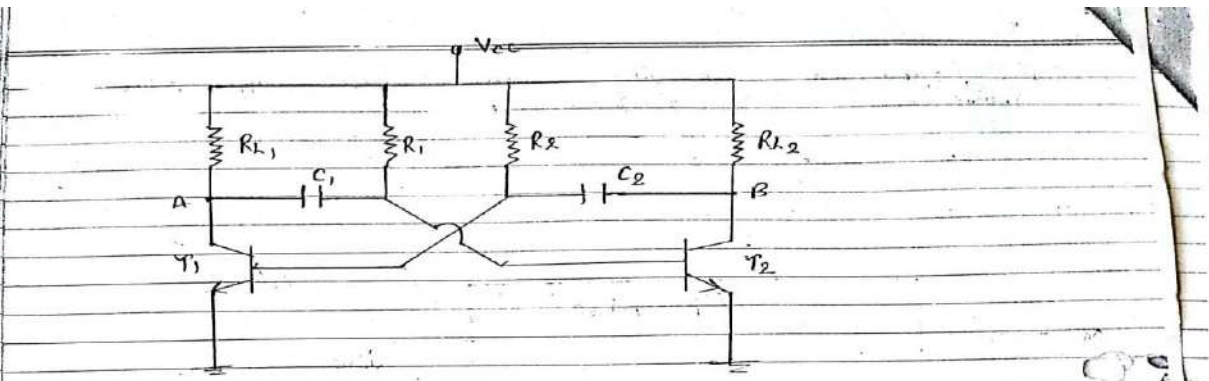c) Astable multivibrator →
Astable multivibrator or free running multivibrator is a device which generate square wave of its own without any external triggering pulse. There is no stable state of course there are two quasi-stable state in one quasi-stable state, one transistor on state and the other being in off state for same time. After this time, in the second quasi-stable state, the second transistor automatically turned on while the first transistor automatically off.



- i) when the transistor T_1 is in saturation, the whole V_{cc} drops across R_1 and transistor T_2 is in cut off it conduct no current.
 - ii) the condensers C_1 start charging R_1 towards V_{cc} . When the volt. across C_1 became more than $0.7V$ the transistor T_2 is F.B. and start conducting.
 - iii) After few cycles, the transistor T_2 is in saturation while the transistor T_1 become cut off.
 - iv) the condensers C_2 start charging through R_2 to potential V_{cc} . When the volt. across C_2 is more than $0.7V$, the transistor T_1 is F.B. and start conducting.
- The on time of transistor T_1 / off time of transistor T_2 →

$$t_1 = 0.69 R_1 C_1$$

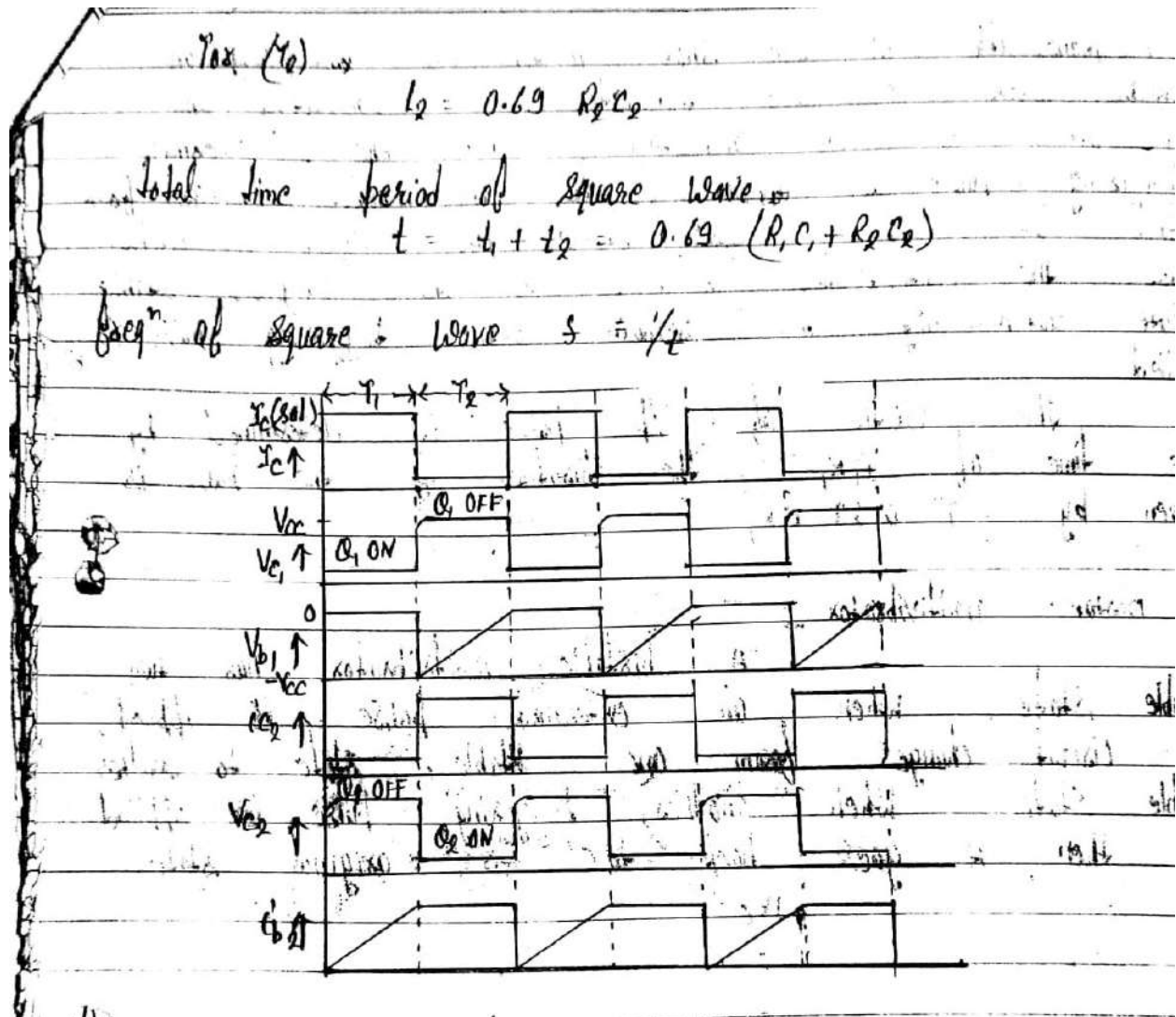

SOLUTION-3

Solution.

$$A_v = 3000, \quad m_v = 0.01$$

\therefore Voltage gain with negative feedback is

$$A_{vf} = \frac{A_v}{1 + A_v m_v} = \frac{3000}{1 + 3000 \times 0.01} = \frac{3000}{31} = 97$$

OR

SOLUTION -3

Solution. $A_v = 140, A_{vf} = 17.5$

Let m_v be the feedback fraction. Voltage gain with negative feedback is

$$A_{vf} = \frac{A_v}{1 + A_v m_v}$$

or $17.5 = \frac{140}{1 + 140 m_v}$

or $17.5 + 2450 m_v = 140$

$\therefore m_v = \frac{140 - 17.5}{2450} = \frac{1}{20}$

SOLUTION-4

Solution.

$$L_1 = 58.6 \mu\text{H} = 58.6 \times 10^{-6} \text{H}$$

$$C_1 = 300 \text{pF} = 300 \times 10^{-12} \text{F}$$

$$\begin{aligned} \text{Frequency of oscillations, } f &= \frac{1}{2\pi \sqrt{L_1 C_1}} \\ &= \frac{1}{2\pi \sqrt{58.6 \times 10^{-6} \times 300 \times 10^{-12}}} \text{ Hz} \\ &= 1199 \times 10^3 \text{ Hz} = \mathbf{1199 \text{ kHz}} \end{aligned}$$

OR

SOLUTION-4

Solution.

$$R_1 = R_2 = R_3 = R = 1 \text{ M}\Omega = 10^6 \Omega$$

$$C_1 = C_2 = C_3 = C = 68 \text{ pF} = 68 \times 10^{-12} \text{ F}$$

Frequency of oscillations is

$$\begin{aligned} f_o &= \frac{1}{2\pi RC \sqrt{6}} \\ &= \frac{1}{2\pi \times 10^6 \times 68 \times 10^{-12} \sqrt{6}} \text{ Hz} \\ &= \mathbf{954 \text{ Hz}} \end{aligned}$$