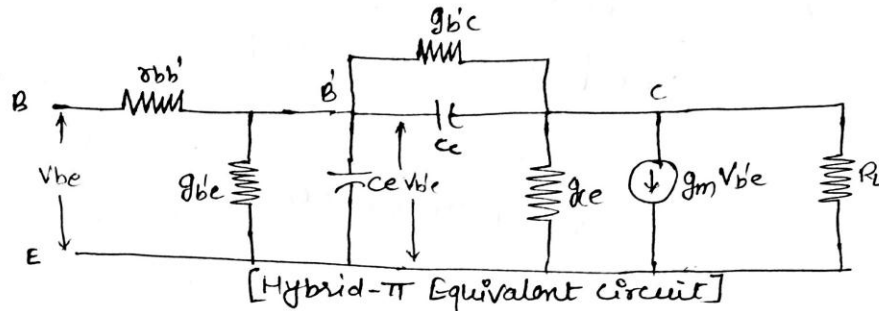


Rajasthan Institute of Technology and Management , Jaipur  
Mid-Term -II solution  
Subject - Analog Electronics  
Semester-4th  
Faculty- Green Maraiya  
Set-A


---
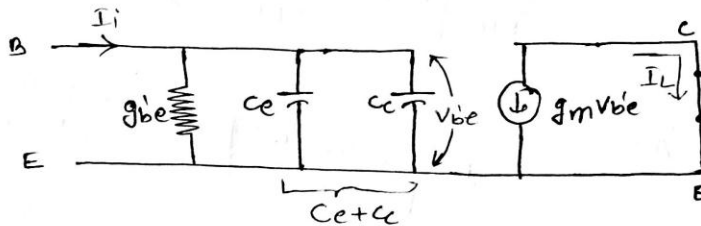
## CE Short circuit current gain



For short circuit current gain and hence it will be assumed  $R_L = 0$  output s.c as result.

- ①  $g_e$  is shorted and becomes zero.
- ② since  $r_{b'c} \gg r_{b'e}$  (therefore  $g_{b'c} \ll g_{b'e}$  hence  $g_{b'c}$  is neglected in comparison with  $g_{b'e}$



$$I_L = -g_m V_{b'e} \quad \text{--- (1)}$$

KCL at input side.

$$I_i = \frac{V_{b'e}}{1/g_{be}} + \frac{V_{b'e}}{j\omega(c_e + c_c)}$$

$$I_i = V_{b'e} [g_{be} + j\omega(c_e + c_c)] \quad \text{--- (2)}$$

Current gain under short circuit

$$A_I = \frac{I_L}{I_i}$$

$$A_I = \frac{-g_m v_{b'e}}{v_{b'e} [g_{b'e} + j\omega (c_e + c_c)]}$$

$$A_I = \frac{-g_m}{g_{b'e} + j\omega (c_e + c_c)} \quad \text{--- (3)}$$

we know  $\therefore g_{b'e} = \frac{g_m}{h_{fe}}$

$$A_I = \frac{-g_m}{g_{b'e} \left[ \frac{g_m}{h_{fe}} + j\omega (c_e + c_c) \right]}$$

$$A_I = \frac{-g_m}{\frac{g_m}{h_{fe}} \left[ 1 + j\omega (c_e + c_c) \frac{h_{fe}}{g_m} \right]}$$

$$A_I = \frac{-h_{fe}}{1 + \left[ \frac{j\omega (c_e + c_c) h_{fe}}{g_m} \right]} = \frac{-h_{fe}}{1 + \left[ \frac{j 2\pi f (c_e + c_c)}{f_{\beta}} \right]}$$

$$A_I = \frac{-h_{fe}}{1 + j \left( \frac{f}{f_{\beta}} \right)} \quad \text{--- (4)}$$

$$f_{\beta} = \frac{g_m}{2\pi (c_e + c_c) h_{fe}} = \frac{g_m}{h_{fe} 2\pi (c_e + c_c)} \quad \text{--- (5)}$$

$$|A_I| = \frac{h_{fe}}{\sqrt{1 + \left( \frac{f}{f_{\beta}} \right)^2}}$$

At  $f = f_p$

$$A_1 = \frac{h_{fe}}{\sqrt{2}}$$

$\beta$ -Cut-off frequency:

$f_p$  is defined as the frequency at which CE s.c current gain falls  $\frac{1}{\sqrt{2}}$  (or 0.707 or fall by 3dB) of its low frequency current gain value i.e  $h_{fe}$  the value of  $f_p$  is

$$f_p = \frac{g_{be}}{2\pi(C_c + C_e)}$$

unity gain frequency ( $f_T$ )

Frequency  $f_T$  is defined as the frequency at which CE s.c current gain becomes unity.

At  $f = f_T$

$$A_1 = 1 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f_T}{f_p}\right)^2}}$$

$$\frac{f_T}{f_p} \gg 1$$

$$1 = \frac{h_{fe}}{\left(\frac{f_T}{f_p}\right)^2}$$

$$\frac{f_T}{f_p} = h_{fe}$$

$$f_T = h_{fe} \cdot f_p$$

$f_T$  represent the CE s.c current gain-bandwidth product.

$$f_T = h_{fe} \cdot f_{\beta}$$

$$f_{\beta} = \frac{f_T}{h_{fe}}$$

from eq (5)


$$\frac{f_T}{h_{fe}} = \frac{g_m}{h_{fe} 2\pi (C_e + C_c)}$$

$$f_T = \frac{g_m}{2\pi (C_e + C_c)}$$

$C_e \gg C_c$

$$f_T = \frac{g_m}{2\pi C_e}$$

current Gain versus frequency curve

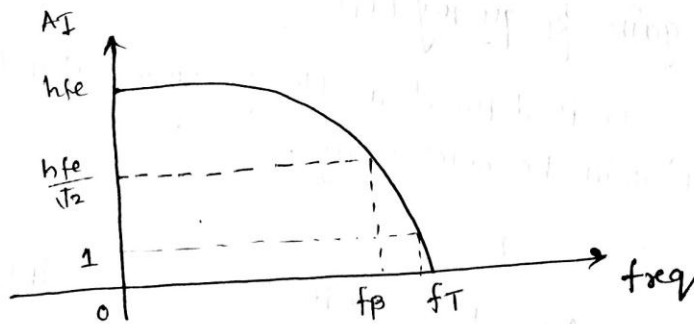

## Ques-1

Solution

$$i) g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}}$$
$$= 38.46 \text{ mA/V}$$

$$ii) r_{b'e} = \frac{h_{fe}}{g_m} = \frac{200}{38.46 \times 10^{-3}}$$
$$= 5.2 \text{ k}\Omega$$

$$iii) (C_e + C_c) = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$
$$= \frac{38.46 \times 10^{-3}}{500 \times 10^6}$$

$$C_e + C_c = 76.92 \text{ PF}$$

$$C_{b'e} = C_e = 76.92 \text{ PF} - 3 \text{ PF} = 73.92 \text{ PF}$$

(iv)

$$f_T = h_{fe} \cdot f_\beta$$

$$2\pi f_T = h_{fe} 2\pi f_\beta$$

$$\omega_T = h_{fe} \omega_\beta$$


$$\omega_\beta = \frac{\omega_T}{h_{fe}} = \frac{500 \times 10^6}{200}$$

$$\omega_\beta = 2.5 \text{ M rad/sec}$$

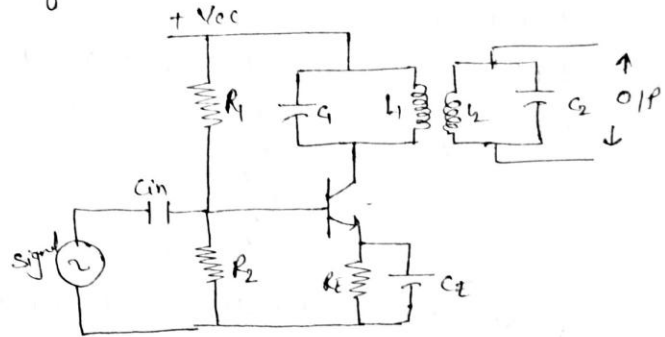
**Ques-2**

Double-tuned Amplifiers

It consists of a transistor amplifier containing two tuned circuits one ( $L_1C_1$ ) in the collector and the other ( $L_2C_2$ ) in the output. The high frequency signal to be amplified is applied to the input terminals of the amplifier. The resonant frequency of tuned circuit ( $L_1C_1$ ) is made equal to the signal frequency. Under such condition the tuned circuit offers very high impedance to the signal frequency. Consequently large output appears across the tuned circuit  $L_1C_1$ . The output from this tuned circuit is transferred to the second tuned circuit  $L_2C_2$  through mutual inductance. Double tuned circuits are extensively used for coupling the various circuits of radio and television receivers.



Frequency response:- The frequency response of a double tuned circuit depends upon the degree of coupling i.e. upon the amount of mutual inductance b/w the two tuned circuits when coil  $L_2$  is coupled to  $L_1$  a portion of load resistance is coupled into the primary tank ckt  $L_1C_1$  and affect the primary ckt in exactly the same manner as though a resistor had been added in series with the primary coil  $L_2$ .

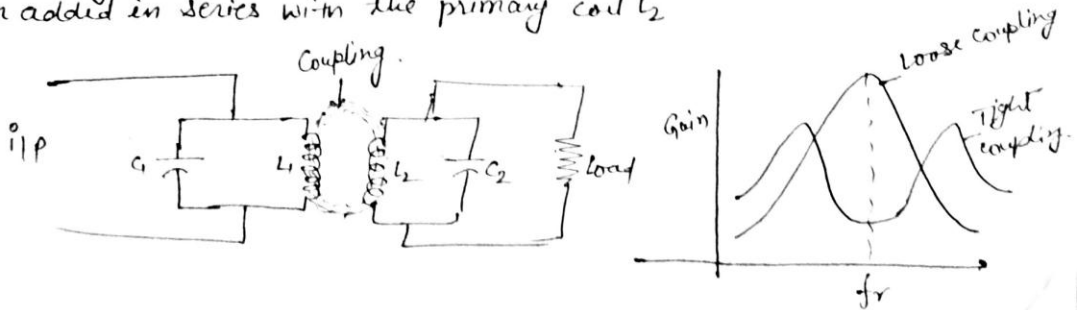

When the coils are spread apart, all the primary coil  $L_1$  flux will not link the secondary coil  $L_2$ . The coils are said to have loose coupling. Under such condition the resistance reflected from the load (i.e. secondary circuit) is small. The resonance curve will be sharp and the circuit Q is high. When primary and secondary coils are very close together, they are said to have tight coupling. Under such conditions, the reflected resistance will be large and the circuit Q is lower.

### Bandwidth of double tuned circuit

BW increase with degree of coupling, determining factor in a double tuned circuit is not Q but the coupling. For given frequency; the lighter the coupling, the greater is BW.

$$BW = k f r$$


$k$  = coefficient of coupling.

### Advantages of double tuned Amplifier.

- 1) BW is increased
- 2) sensitivity (i.e. ability to receive weak signal) is increased
- 3) selectivity (i.e. " to discriminate against signal in adjacent bands) is increased.




## Stagger tuned Amplifier

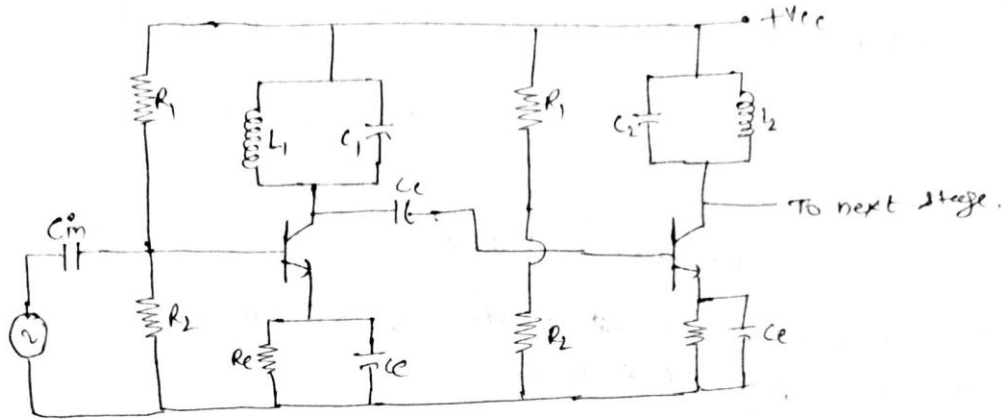

If two or more tuned circuits are cascaded and tuned to the same frequency; thus the overall bandwidth decreases it is known as synchronous tuning.

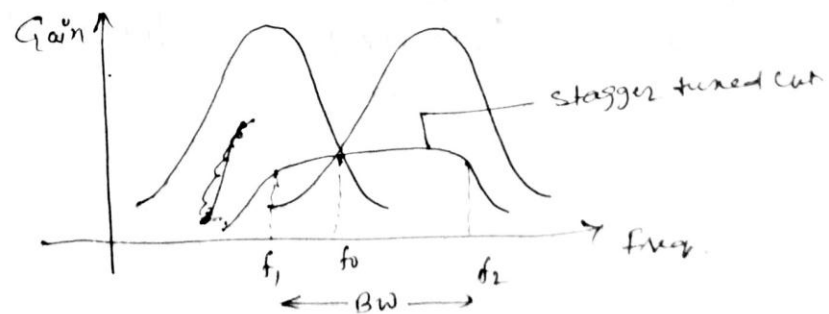If the tuned are cascaded and they are tuned to different frequencies it is possible to obtain increased bandwidth with more desirable bandpass char. i.e flat pass band with steep sides. This technique is called stagger-tuning.



Amplifier has a greater BW and flatter top pass band if more number of stages are used flatter will be the passband and steeper will be the gain fall-off outside the passband.

Analysis the gain of tuned-circuit amplifiers is given by

$$\frac{A_v}{(A_v \text{ at resonance})} = \frac{1}{1 + j2Qs} = \frac{1}{1 + jx} \quad x = 2Qs$$

Since one stage is tuned at the frequency below and other above to the corresponding selectivity is

$$\left( \frac{A_v}{A_v \text{ at resonance}} \right) = \frac{1}{1 + j(x-1)} \quad \text{--- (1)}$$

$$\left( \frac{A_v}{A_v \text{ at resonance}} \right) = \frac{1}{1 + j(x+1)} \quad \text{--- (2)}$$



$$1 \times 2 = \frac{1}{1 + j(x-1)} \times \frac{1}{1 + j(x+1)} = \frac{1}{2 - x^2 + j2x}$$

$$| \text{gain} | = \frac{1}{\sqrt{(2 - x^2)^2 + (2x)^2}} = \frac{1}{\sqrt{4 + x^4}}$$

$$\boxed{ | \text{gain} | = \frac{1}{\sqrt{4 + (2Qs)^4}} = \frac{1}{2} \frac{1}{\sqrt{1 + 4Q^4 s^4}} }$$

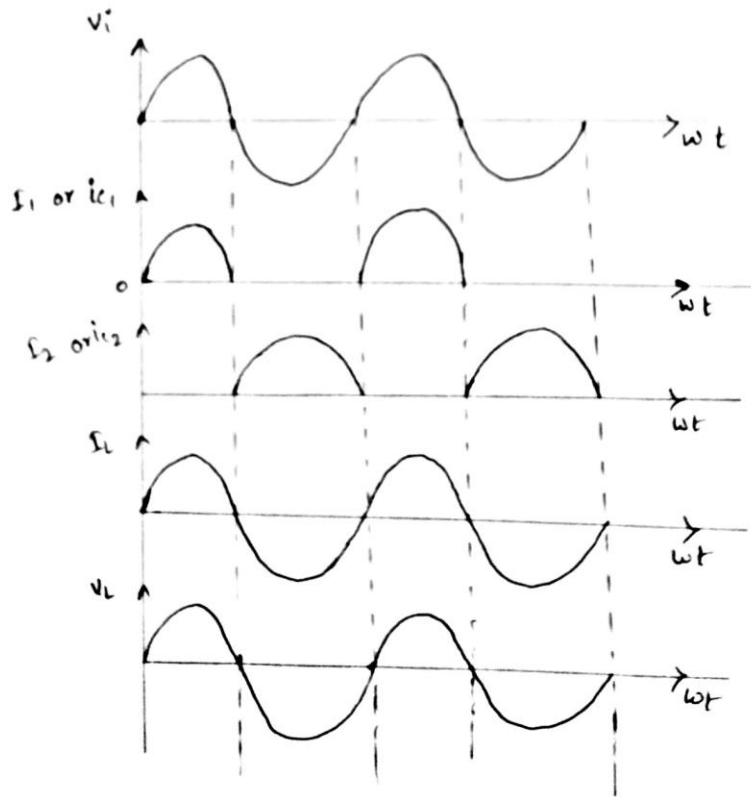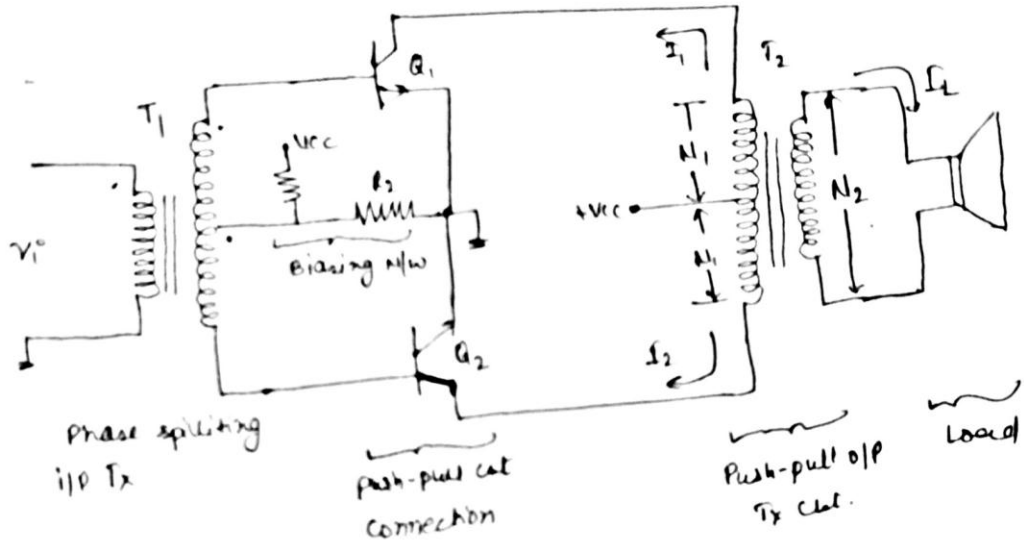**Ques-3**

Draw the circuit diagram and explain the operation with relevant waveforms of class-B push-pull amplifiers. Also show that the maximum conversion efficiency of class-B push-pull amplifier is 78.5%.



The dc biasing point i.e. Q point is adjusted on the x-axis such that  $V_{CEQ} = V_{CC}$  and  $I_{CQ} = 0$

→ Hence co-ordinates of the Q point are  $(V_{CC}, 0)$

DC ~~output~~ power

→ Each transistor o/p is in the form of half rectified sinusoid with a peak value of  $I_m$  or  $I_{CP}$

→ Thus the average current in each transistor is  $\frac{I_m}{\pi}$

→ Since, there are two transistor, the dc current drawn from the supply  $V_{CC}$ , by both the transistor is

$$I_{DC} = 2 \times (\text{Average current in each transistor})$$

$$I_{DC} = \frac{2 \times I_m}{\pi}$$

∴ The DC i/p power

$$P_{i(DC)} = V_{CC} \cdot I_{DC}$$

$$= V_{CC} \cdot \left( \frac{2 I_m}{\pi} \right)$$

$$P_{i(DC)} = \frac{2}{\pi} \times V_{CC} \cdot I_m$$


AC operation

The AC power is

$$P_{AC} = V_{rms} \cdot I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$P_{AC} = \frac{V_m \cdot I_m}{2}$$

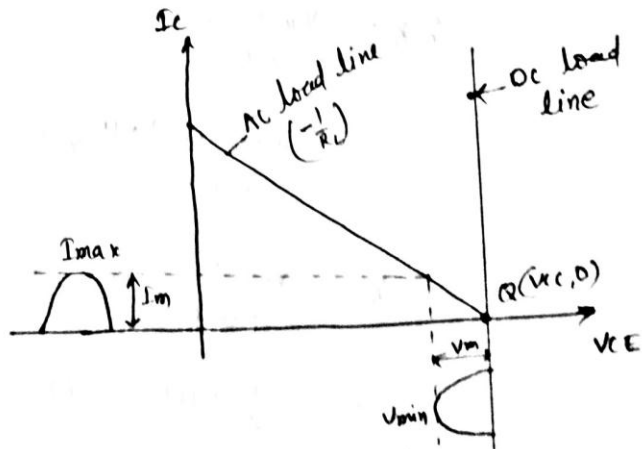

$$P_{ac} = \frac{V_m}{2} \cdot \frac{V_m}{R'_L}$$

$$P_{ac} = \frac{V_m^2}{2R'_L}$$

or

$$P_{ac} = I_m \cdot R'_L \cdot \frac{I_m}{2}$$

$$P_{ac} = \frac{I_m^2 \cdot R'_L}{2}$$

efficiency :-

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100$$

$$= \frac{\frac{V_m \cdot I_m}{2}}{\frac{V_{CC} \cdot 2I_m}{\pi}} \times 100$$

$$= \frac{V_m}{2} \times \frac{1}{2V_{CC}} \times 100$$

$$\% \eta = \frac{V_m \cdot \pi}{4V_{CC}} \times 100$$

Maximum efficiency :-


$V_m = V_{CC}$  - For max efficiency

$$\% \eta = \frac{V_m \cdot \pi}{4V_{CC}} \times 100$$

$$= \frac{(V_{max} - V_{min}) \cdot \pi}{4V_{CC}} \times 100$$

$$\% \eta = \frac{V_{CC} \cdot \pi}{4V_{CC}} \times 100$$
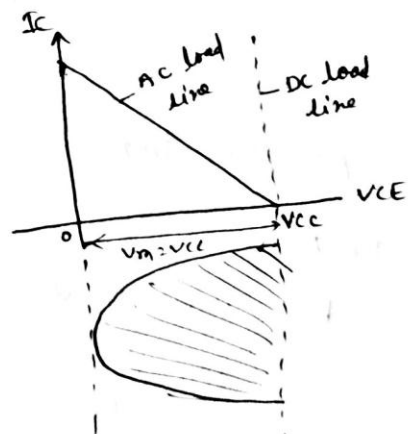
$$\% \eta = \frac{\pi}{4} \times 100 = 78.5\%$$



### Ques-3

Solve  $V_{CC} = 10V$   $R_L = 16\Omega$  overall  $\eta =$  collector  $\eta = 0.5$   
 $P_{tr} = 100mW$

(i) output power a.c

$$\text{collector efficiency} = \frac{(P_o)_{ac}}{P_{tr}}$$

$$0.5 = \frac{(P_o)_{ac}}{100mW}$$

$$(P_o)_{ac} = 0.5 \times 0.1 = 0.05 \text{ watts.}$$

(ii) output power ac is given by

$$(P_o)_{ac} = \frac{1}{2} V_{CC} \cdot I_{cA}$$

$$0.05 = \frac{1}{2} \times 10 \times I_{cA}$$

$$0.05 = \frac{1}{2} 5 \times I_{cA}$$

$$I_{cA} = \frac{0.05}{5} = 0.01A$$

(iii) Transformer turns ratio

$$R_L' = N^2 R_L$$

$$R_L' = \frac{V_{CC}}{I_{cA}} = \frac{10}{0.01} = 1000\Omega$$

$$1000 = N^2 \times R_L$$

$$N = \sqrt{\frac{1000}{16}}$$

$$\boxed{N = 8}$$

### Ques-4(a)

The comparison b/w voltage and power Amplifier.

Parameter	Voltage Amplifier	Power Amplifier
$\beta$	high ( $>100$ )	low (5 to 20)
$R_c$	high (4-10 k $\Omega$ )	low (5 to 20 $\Omega$ )
Coupling	usually R-C coupling	Transformer coupling
Input voltage	low (a few mV)	high (2-4V)
Collector current	low ( $\approx 1\text{mA}$ )	high ( $>100\text{mA}$ )
Power o/p	low	High
output Impedance	High ( $\approx 12\text{ k}\Omega$ )	low (200 $\Omega$ )




## Classification of power Amplifier

- + Class-A power Amplifier
- Class-B
- Class-AB
- Class-C
- Class-D

## Class-A power Amplifier

→ Collector current flows for entire 360° of P/P signal.

Conduction angle =  $2\pi$

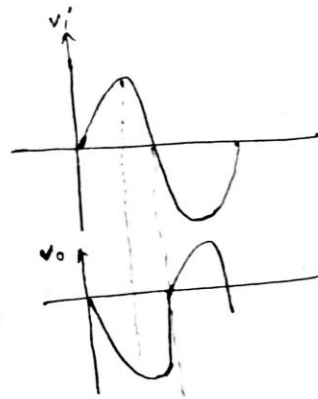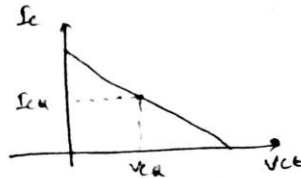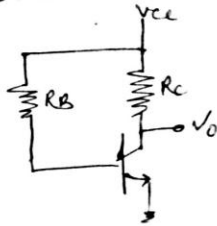

→ Q point is located at centre of dc load line

Advantage :- Minimum distortion

→ Excellent thermal stability i.e., no thermal runaway problem.

Disadvantage :- Small power conversion efficiency


Application :- Designing of audio freq amplifier.

→ In class-A operation, power dissipated by  $T_x$  is equal to max signal power O/P.


For class-A,  $P_D = P_{O \max}$  i.e. max power O/P





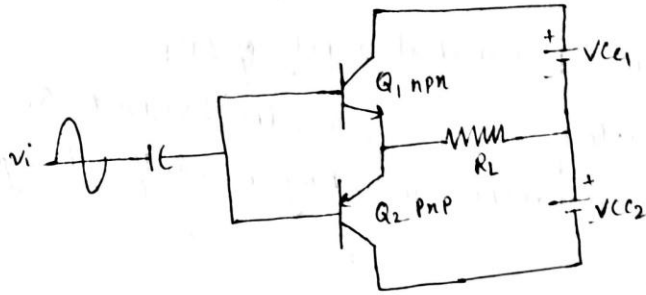
# Complementary Symmetry class-B Amplifier. (Common collector-emitter follower)



(a)

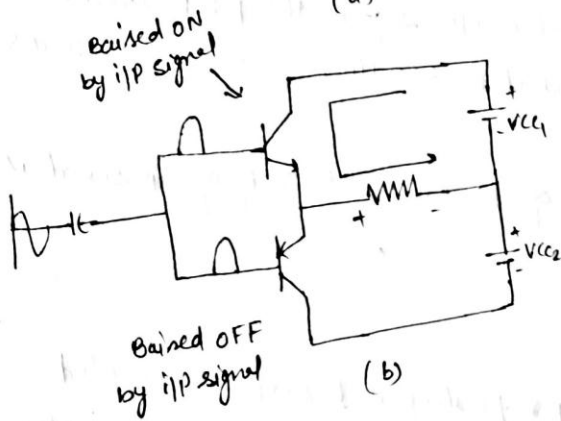

(b)

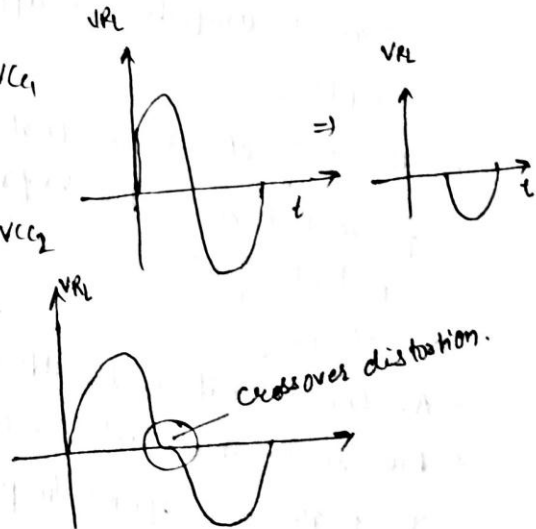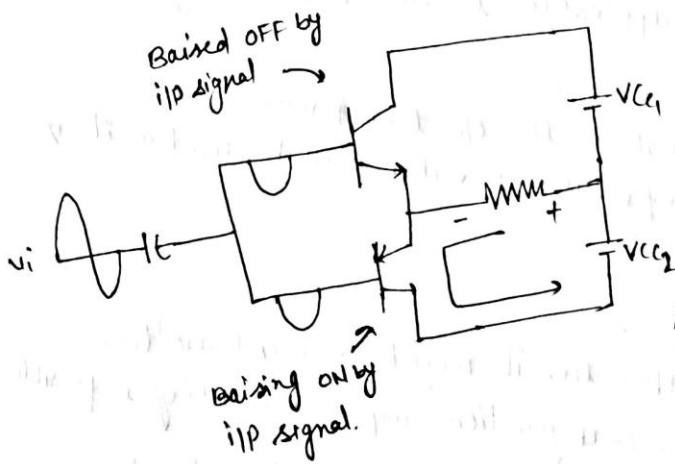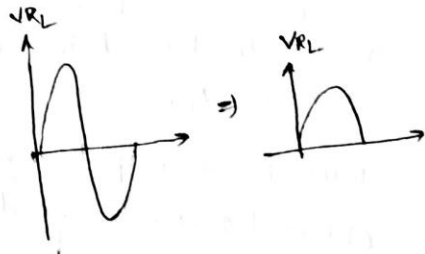

- In Complementary symmetry class-B amplifier, one is n-p-n and the other is p-n-p transistor.
- The transistor  $Q_1$  is n-p-n while  $Q_2$  is p-n-p type
- The circuit is driven from a dual supply of  $\pm V_{CC}$
- During +ve half cycle of the i/p signal, the transistor  $Q_1$  will be biased into conduction, resulting in a half cycle signal across the load
- During -ve half cycle of the i/p signal the p-n-p transistor  $Q_2$  will be biased into conduction resulting in -ve half cycle across the load  $R_L$ .
- Thus for a complete cycle of i/p a complete cycle of o/p signal is obtained across the load.

### Mathematical Analysis:

- All the result derived for push-pull transformer coupled class-B amplifier are applicable to the complementary class-B amplifier.
- The only change is that as the o/p transformer is not present hence in the expression,  $R_L$  value must be used as it is instead of  $R_L'$

### Advantages :-

- As the circuit is transformerless. its weight, size & cost are less
- Due to common collector configuration, impedance matching is possible.
- The frequency response improves due to transformerless class-B amplifier ckt.


---

Rajasthan Institute of Technology and Management, Jaipur  
Mid-Term-II Solution  
Subject- Analog Electronics  
Semester-4th  
Faculty- Green Maraiya  
Set-B

---

## Question-1

### Hybrid- $\pi$ Model

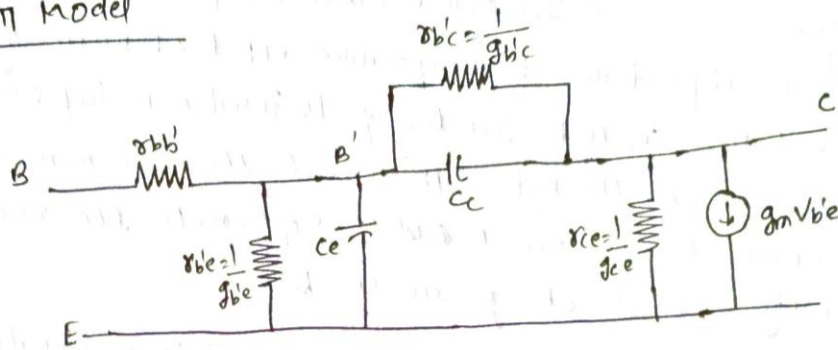

$r_{bb'}$  = Ohmic base spreading resistance

$r_{ce}$  = Early effect

$r_{be}$  = Forward junction resistance

$r_{bc}$  = show early effect for  $J_c$  Junction (high)

$g_m$  = Transconductance  $\boxed{g_m = \frac{|I_c|}{V_T}}$

$r_{bb'}$  - Base region of transistor is very thin compared to emitter & collector region & its resistance lies b/w 40 to 400  $\Omega$ . The ohmic resistance of E and C is usually of order of 10  $\Omega$  and can be neglected in comparison to that of base region.

$r_{be}$  - Incremental resistance of E-B diode which is FB in active region.

$r_{bc}$  - It accounts for feedback from o/p to i/p due to base width modulation or early effect. The value of  $r_{bc}$  is usually very high (several M $\Omega$ ) and will be neglected in analysis.

see :- o/p resistance and it is also due to Early effect

### The hybrid Capacitance

Forward biased PN Junction exhibits a capacitive effect called diffusion capacitance. This capacitive effect of normally forward biased base-emitter junction of transistor is represented by  $C_{bc}$  or  $C_{be}$  in the hybrid- $\pi$  model the diffusion capacitance  $C_e$  connected between B and E represents the excess minority carrier storage in the base.

The reverse biased PN Junction exhibits a capacitive effect called transition capacitance. The capacitive effect of normally reverse biased collector base junction of the transistor represented by  $C_{bc}$  or  $C_{cc}$  in the hybrid- $\pi$  model.

## High frequency Response of Emitter follower

$$V_{BE} = 0.7 \text{ for Si}$$
$$= 0.3 \text{ for Ge}$$

RCL

$$V_{BE} + V_o - V_i = 0$$

$$V_{BE} - V_i = -V_o$$

$$V_o = V_i - V_{BE}$$

if  $V_i = 40$

$$V_o = 40 - 0.7$$

$$V_o = 39.3V \text{ for Si}$$


$$V_o = 40 - 0.3$$

$$= 39.7V \text{ for Ge}$$


So,  $V_o \approx V_i$

$$\text{gain} = \frac{V_o}{V_i} = A_v$$

$$A_v \approx 1$$

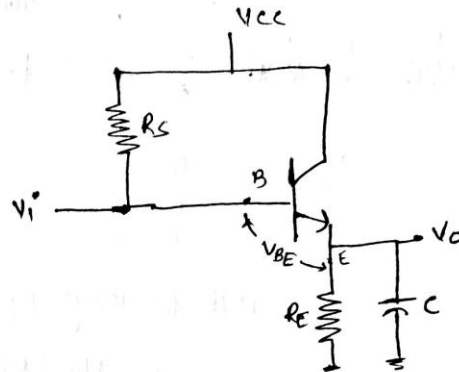


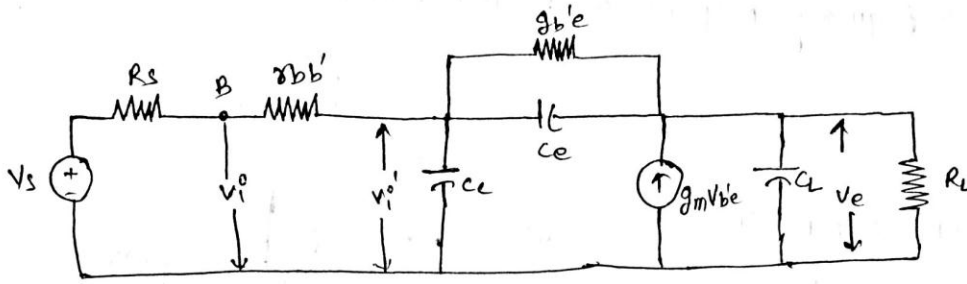The circuit of emitter follower at high frequency is described using fig a Capacitive  $C_L$  is included across the resistor  $R_E$  because the emitter follower due to its low O/P impedance is often used to drive capacitive load,  $C_L$  represents the shunt capacitance of capacitive load.




High frequency equivalent circuit.

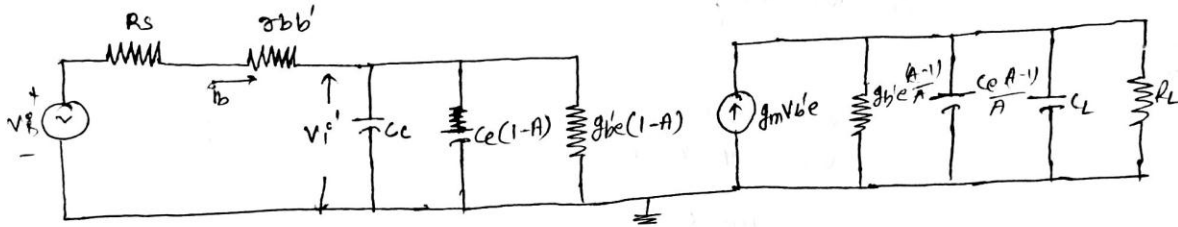Apply Miller's theorem to the hybrid  $\pi$ -model.



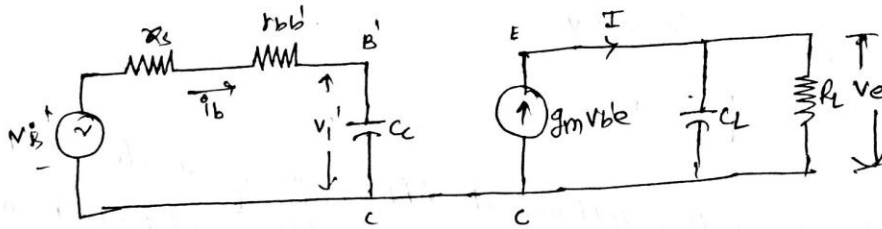We know that, the freq of an emitter follower is very close to unit  
 $\therefore (A \approx 1)$



$$V_e = I \times Z$$

$$V_e = I \times \left( R_L \times \frac{1}{j\omega C_L} \right) / \left( R_L + \frac{1}{j\omega C_L} \right)$$

$$V_e = g_m V_{be} \times R_L / (1 + j\omega C_L R_L)$$

$$V_e = \frac{g_m \cdot R_L}{1 + j\omega C_L R_L} \cdot V_{be}$$

$$v_e = \frac{g_m \cdot R_L}{1 + j\omega C_L R_L} (v_i' - v_e)$$

$$v_e = \frac{g_m \cdot R_L \cdot v_i'}{1 + j\omega C_L R_L} - \frac{g_m \cdot R_L v_e}{1 + j\omega C_L R_L}$$

$$v_e \left( 1 + \frac{g_m R_L}{1 + j\omega C_L R_L} \right) = \frac{g_m R_L \cdot v_i'}{1 + j\omega C_L R_L}$$

$$v_e \left( \frac{1 + j\omega C_L R_L + g_m R_L}{1 + j\omega C_L R_L} \right) = \frac{g_m \cdot R_L \cdot v_i'}{1 + j\omega C_L R_L}$$

$$\frac{v_e}{v_i'} = \frac{g_m R_L}{1 + g_m R_L + j\omega C_L R_L}$$

$$\frac{v_o}{v_i} = \frac{v_e}{v_i'} = \frac{g_m R_L}{(1 + g_m R_L) \left[ 1 + \left( \frac{j\omega C_L R_L}{1 + g_m R_L} \right) \right]}$$

$$\frac{v_o}{v_i} = \frac{\frac{g_m R_L}{1 + g_m R_L}}{1 + \frac{j\omega C_L R_L}{1 + g_m R_L}}$$

$$\frac{v_o}{v_i} = \frac{g_m R_L}{1 + g_m R_L} \times \frac{1}{1 + j \left( \frac{f}{f_H} \right)}$$

$$A_v = \frac{A_o}{1 + j \left( \frac{f}{f_H} \right)}$$

$$A_o = \frac{g_m R_L}{1 + g_m R_L} \approx 1 \text{ (Gain)}$$



$$f_H = \frac{1 + g_m R_L}{2\pi C_L R_L}$$

Now, since the input impedance between terminal B and C is very large in comparison ( $r_{bb} + R_S$ ) so overall voltage gain

$$A_{vs} = \frac{v_o}{v_i} = \frac{A_o}{1 + j \frac{f}{f_H}}$$


$f_H \rightarrow$  High cut-off freq

## Ques-2

Transformer coupled class-A power Amplifier.

or

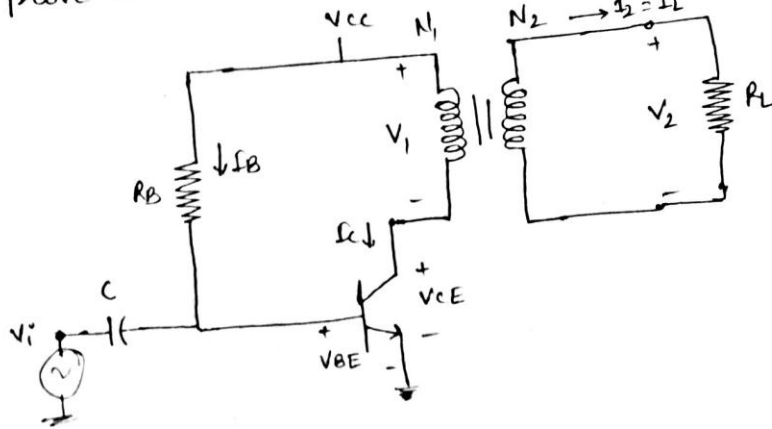prove that the maximum power efficiency is 50%.



### DC operation

- It is assumed that the winding resistances are zero ohms
- There is no dc voltage drop across primary of transformer w.k.t the slope of dc load line is reciprocal of the dc resistance in the collector ckt ( $\frac{1}{R_{dc}} = \frac{1}{0} = \infty$ )

Applying KVL to the collector ckt.


$$V_{CC} - V_{CE} = 0$$

$$V_{CC} = V_{CE}$$

$$V_{CEQ} = V_{CC}$$

This is the dc bias voltage  $V_{CEQ}$  for the transistor.

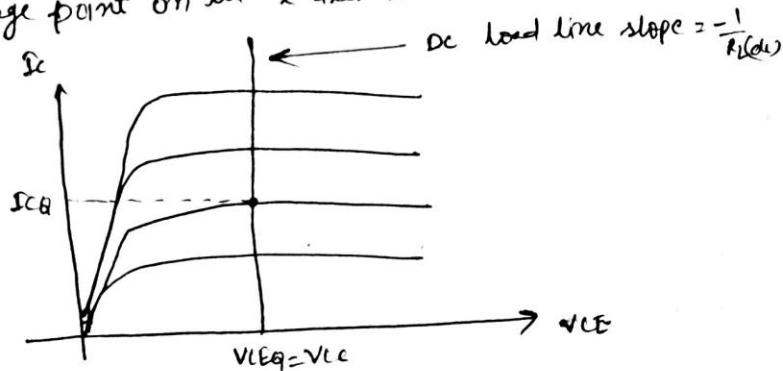- Hence the dc load line is a vertical straight line passing through a voltage point on the x-axis which is  $V_{CEQ} = V_{CC}$



Similarly, the ac power delivered to the load on secondary can be calculated using secondary quantities.

let  $V_{2m}$  = peak value of secondary or load voltage  
 $I_{2m}$  = peak value of secondary or load current.


$$P_{ac} = \frac{V_{2m} \cdot I_{2m}}{2}$$

$$P_{ac} = \frac{(V_{max} - V_{min}) \cdot (I_{max} - I_{min})}{8}$$

Efficiency %:


$$\eta = \frac{P_{ac}}{P_{dc}} \times 100$$
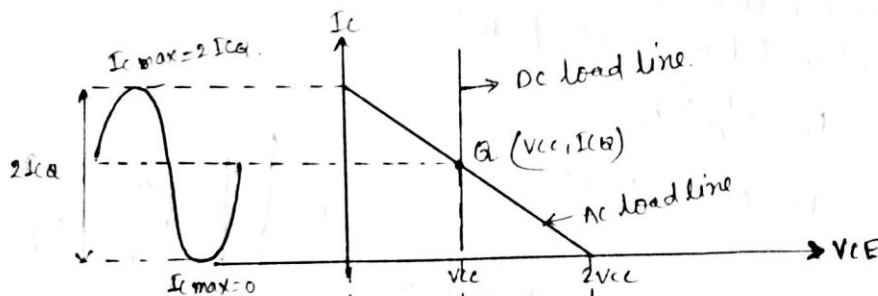
$$\eta = \frac{(V_{max} - V_{min}) \cdot (I_{max} - I_{min}) \times 100}{8 V_{CC} \cdot I_{CQ}}$$



$$V_{max} = 2V_{CC} ; V_{min} = 0$$

$$I_{cmax} = 2I_{CQ} ; I_{cmin} = 0$$

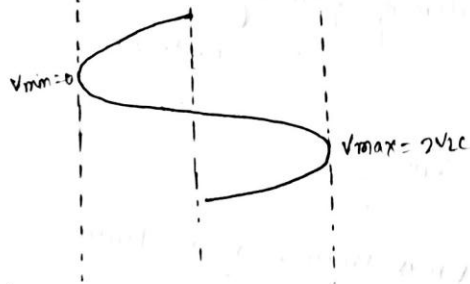

$$\eta = \frac{(2V_{CE}) (2I_{CQ})}{8 V_{CC} \cdot I_{CQ}} = \frac{1}{4} = 50\%$$

$$\eta = 50\%$$

### Ques-3


parallel resonance (parallel LC circuit)

- Circuit current is in phase with voltage applied.
- phase angle  $\phi$  b/w current and voltage is zero.
- The circuit is resistive in nature.
- power factor  $(\cos \phi) = 1$

Resonant frequency

$$X_L = 2\pi fL \text{ (Inductive reactance)}$$
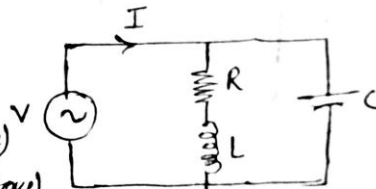
$$X_C = \frac{1}{2\pi fC} \text{ (Capacitive reactance)}$$



$$Z_1 = R + jX_L$$

$$Y_1 = \frac{1}{R + jX_L} \text{ (admittance)}$$

$$= \frac{1}{R + jX_L} \times \frac{R - jX_L}{R - jX_L} = \frac{R - jX_L}{R^2 + X_L^2}$$

$$Y_1 = \frac{R}{R^2 + X_L^2} - \frac{jX_L}{R^2 + X_L^2} \quad \text{--- (1)}$$

$$Z_2 = -jX_C$$

$$Y_2 = \frac{1}{-jX_C} = \frac{j}{X_C} \quad \text{--- (2)}$$

Total admittance

$$Y_T = Y_1 + Y_2$$

$$= \frac{R}{R^2 + X_L^2} - \frac{jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$Y_T = \frac{R}{R^2 + X_L^2} + j \left( \frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} \right)$$

At resonance

imaginary part of  $Y_T$  is zero.

$$R_T = \frac{R}{R^2 + X_L^2}$$

$$\frac{1}{X_C} - \frac{X_L}{R^2 + X_L^2} = 0$$

$$\frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

$$\Rightarrow X_L X_C = R^2 + X_L^2$$

$$2\pi f_r L \cdot \frac{1}{2\pi f_r C} = R^2 + (2\pi f_r L)^2$$

$$\frac{L}{C} = R^2 + 4\pi^2 f_r^2 L^2$$

$$\frac{L}{C} - R^2 = (4\pi^2 L^2) \cdot f_r^2$$

$$f_r = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{L}{C} - R^2}$$

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Dynamic resistance

At resonance

$$Y_T = \frac{R}{R^2 + X_L^2}$$

$$\text{impedance} = R_D = \frac{1}{Y_T} = \frac{R^2 + X_L^2}{R}$$

$$Z_T = \frac{Z_L^2}{R}$$

$$Z_T = \frac{4L}{R}$$

$$Z_T = \frac{L}{CR}$$

dynamic resistance

$$Z_1 = R + j\omega L \quad Z_2 = \frac{1}{j\omega C}$$

$$R + j\omega L \cdot \frac{1}{j\omega C}$$


$$R + j\omega L - \frac{1}{\omega C}$$

At parallel resonance

→ Admittance decrease. i.e Impedance ↑.

→ Current decrease.

→ This ckt is rejector circuit.

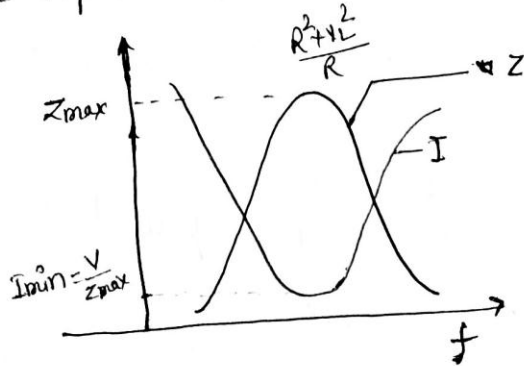


Ideal tank ckt

$$Y_T = Y_L + Y_C$$

$$Z_L = jX_L ; Z_C = \frac{1}{j\omega C} = -jX_C$$

$$Y_L = \frac{1}{jX_L} ; Y_C = \frac{j}{X_C}$$
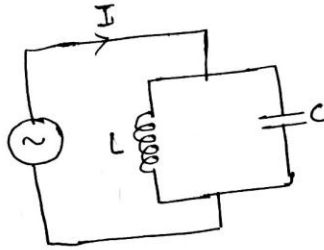
$$Y_T = j \left[ \frac{1}{X_C} - \frac{1}{X_L} \right]$$



At resonance

$$\frac{1}{X_C} - \frac{1}{X_L} = 0$$

$$\frac{1}{X_C} = \frac{1}{X_L} \Rightarrow$$

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r^2 = \frac{1}{(2\pi)^2 LC}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

### Ques-4

Solution i)

$$g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}}$$

$$= 38.46 \text{ mA/V}$$

$$\text{ii) } r_{be} = \frac{h_{fe}}{g_m} = \frac{200}{38.46 \times 10^{-3}}$$

$$= 5.20 \text{ k}\Omega$$

$$\text{iii) } (C_e + C_c) = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$

$$= \frac{38.46 \times 10^{-3}}{500 \times 10^6}$$

$$C_e + C_c = 76.92 \text{ PF}$$

$$C_{be} = C_e = 76.92 \text{ PF} - 3 \text{ PF} = 73.92 \text{ PF}$$

(iv)

$$f_T = h_{fe} \cdot f_\beta$$

$$2\pi f_T = h_{fe} 2\pi f_\beta$$

$$\omega_T = h_{fe} \omega_\beta$$

$$\omega_\beta = \frac{\omega_T}{h_{fe}} = \frac{500 \times 10^6}{200}$$

$$\boxed{\omega_\beta = 2.5 \text{ M rad/sec}}$$

## Unit-5

Green Malaya  
M.Tech Nit Rowreds.  
Ph-9981533280

### Power Amplifier


- It is last stage of multi-stage Amplifier
- power Amplifier is defined as ability of amplifier to convert available o/p dc power into ac signal power with the amplification of i/p signal.
- Transistors used in power Amplifier are called, transistor <sup>power</sup>
- power Amplifier are designed mostly by BJT & they are generally in CE mode.

### Small signal Amplifier

- i/p signal amplitude are very small ( $\mu V$  or  $mV$ )
- operate only in linear region
- Important specification  $A_I, A_v, R_i, R_o, \phi$
- Analysis amp will be done using graphical as well as mathematical.
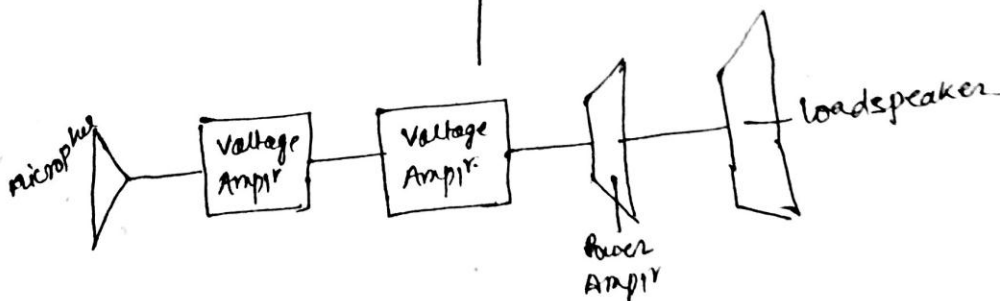
### Large Signal Amplifier

- i/p signal amplitude are very high ( $V, 10V$ )
- operate only both in linear and Non-linear region of i/p char. curve.
- Important specification are:
  - power conversion efficiency  $\eta$
  - DC power available at o/p
  - by only graphical analysis.





The comparison b/w voltage and power Amplifiers.

Parameter	Voltage Amplifier	Power Amplifier
$\beta$	high ( $>100$ )	Low (5 to 20)
$R_c$	high (4-10 k $\Omega$ )	low (5 to 20 $\Omega$ )
Coupling	usually R-C coupling	Transformer coupling
Input Voltage	low (a few mV)	high (2-4 V)
Collector Current	low ( $\approx 1$ mA)	high ( $>100$ mA)
Power o/p	low	High
output Impedance	High ( $\approx 12$ k $\Omega$ )	low (200 $\Omega$ )




## Classification of power Amplifier

- + Class-A power Amplifier
- Class-B
- Class-AB
- Class-C
- Class-D

## Class-A power Amplifier

→ Collector current flows for entire 360° of P/P signal.

Conduction angle =  $2\pi$

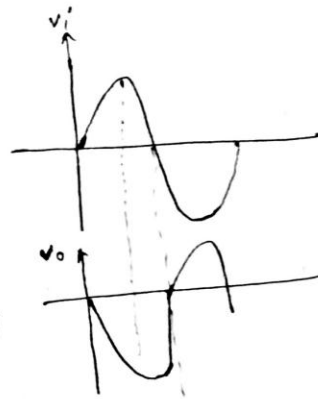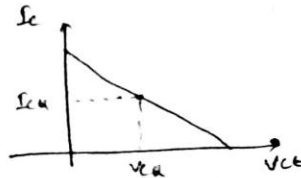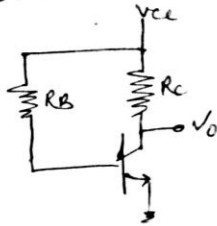

→ Q point is located at centre of dc load line

Advantage :- Minimum distortion

→ Excellent thermal stability i.e., no thermal runaway problem.

Disadvantage :- Small power conversion efficiency



Application :- Designing of audio freq amplifier.

→ In class-A operation, power dissipated by  $T_x$  is equal to max signal power O/P.

For class-A,  $P_D = P_{O \max}$  i.e. max power O/P
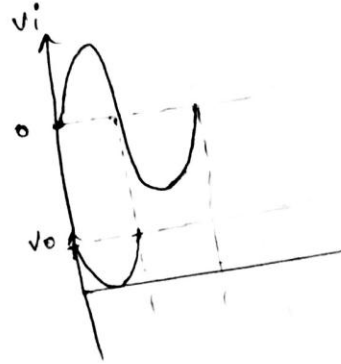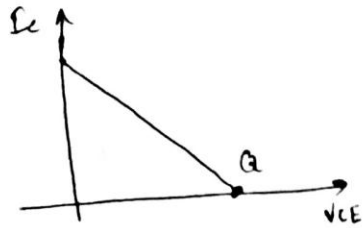
### Class-B operation :-

- collector current flows ~~exactly~~ exactly for 180° of i/p signal
- Q point is located at cut-off.
- It is double ended amplifier i.e. two transistor in one stage.



Advantage :- Higher efficiency (78.5%)  
Power drain is eliminated

Disadvantage :- Higher distortion  
→ Thermal stability is less  
→ Introduce crossover distortion.

Power dissipated by single Tx in Ckt.

$$P_D = 0.2 P_{Omax}$$


Power dissipated by circuit i.e. 2Tx

$$P_D = 0.4 P_{Omax}$$

For e.g. :- To design a class-B amplifier with 20W o/p signal power, Tx must dissipate <sup>4W</sup> 20W of Pow.
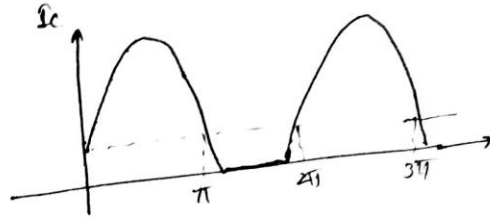
### Class-AB power Amplifier :-

- conduction angle  $180^\circ < \phi < 360^\circ$
- A point is located in active region but close to cut-off region
- Distortion & Noise interference is more as compared to class-A & less than compared to class-B.



### Class-C power Amplifier

- conduction angle  $< 180^\circ$

